Answer Sheet

Score:60/60

Raleigh Div. B Invitational 2026

Circuit Lab

School: North Carolina State University

Circle One: Varsity JV1

Team Number:_____

Tiebreakers: [40, 24, 18, 12, 6, 36]

Student Name: Go

Student Name: Pack

Matching (8 pts total)

1. (1 pt)	A
2. (1 pt)	C
3. (1 pt)	H
4. (1 pt)	B
5. (1 pt)	F
6. (1 pt)	G
7. (1 pt)	D
8. (1 pt)	E

Calculations (must include units) (8 pts total)

9. (2 pts)	4.5V (or 4.5 Volts)
10. (2 pts)	5:1
11. (2 pts)	1920W (or 1.92kW or 1920 Watts)
12. (2 pts)	0.12Ω (or 0.12 Ohms or 120mΩ)

Multiple Choice (13 pts total)

13. (1 pt)	B
14. (1 pt)	A
15. (1 pt)	D
16. (1 pt)	B
17. (1 pt)	A
18. (1 pt)	B
19. (1 pt)	A

20. (1 pt)	B
21. (1 pt)	D
22. (1 pt)	B
23. (1 pt)	A
24. (1 pt)	B
25. (1 pt)	C


True or False (12 pts total)

26. (1 pt)	False
27. (1 pt)	True
28. (1 pt)	False
29. (1 pt)	False
30. (1 pt)	True
31. (1 pt)	True
32. (1 pt)	False
33. (1 pt)	True
34. (1 pt)	True
35. (1 pt)	True
36. (1 pt)	True
37. (1 pt)	False

Circuit Analysis (9 pts total)

38. (3 pts)	100Ω (or 100 Ohms or 0.1kΩ)
39. (2 pts)	0.05A (or 50mA or 0.05 Amps)
40. (3 pts)	0.625V (or 625mV or 0.625 Volts)
41. (1 pt)	0.25W (or 0.25 Watts or 250mW)

Lab Configuration (10 pts)

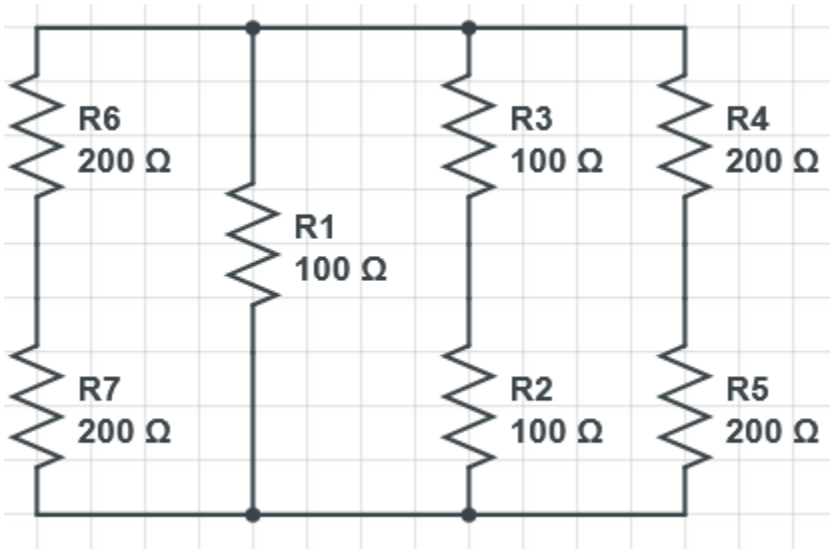

Any combination so long as there are 2 rows with two 200 Ohm resistors, 1 row with two 100 Ohm resistors, and a lone 100 Ohm resistor. All of these rows are in parallel with each other.